

## Learning About Transistor Biasing

Demo Design Specs.:

Vcc = 6

LED = 1.7v @20mA

Driving from Arduino Digital I/O @

5v (40mA max).

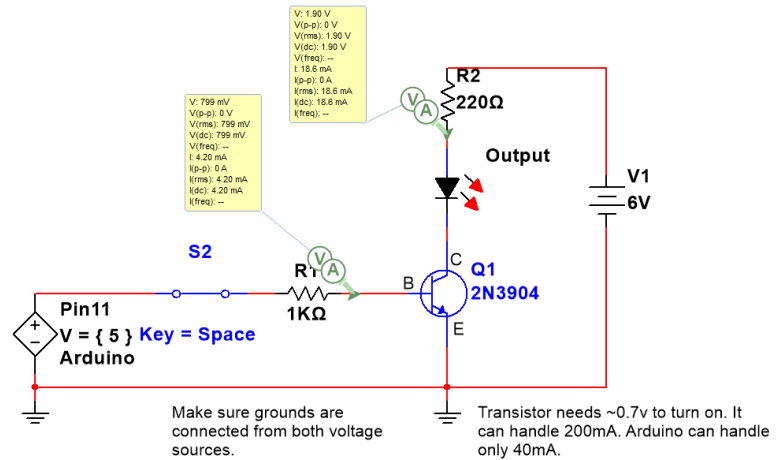


Figure 1: Our circuit in Multisim with the calculated values,

STEP 1: Compute value of our base

resistor ( $R_b$ ). This resistor controls current into the transistor to keep it from burning up. So always use one!

- Design with these specs to drive the transistor into saturation.:
  - The output of the Arduino pin is **5V**.
  - The transistor needs **~.7V** to turn on just like a diode.
  - Let's limit base-emitter current ( $I_{BE}$ ) to **5mA (.005A)** to protect the Arduino.
- Therefore, the base resistor value is:

$$R_b = \frac{5v - .7v}{.005A} = \underline{860\Omega}. \text{ We can use a } \underline{1K\Omega} \text{ because it is a more common value.}$$


- The simulation confirms a base voltage of 799mV (.79V) @ 4.20mA which is within our limit of 5mA when  $R_b = 1K\Omega$ .**

STEP 2: Calculate value for current limiter resistor for the LED.

- According to the datasheet, the voltage from collector to emitter is about ~200mV or .2v when the transistor is saturated or turned on all the way. See table below.
- The LED draws 1.7v and 20mA, the  $V_{ce(sat)} = 0.2v$ , and the  $V_{cc} = 6v$ . So that leaves 4.1v ( $6v - 1.7 - .2v$ ) that the limiting resistor must drop. Therefore:
- $R_{LED} = \frac{4.1v}{.020A} = 205$  so 220Ω is a safe value.
- At 220Ω,  $V_{LED} = 1.9v$  @18.6mA (in Multisim).**

STEP 3: Calculate power rating for  $R_{LED}$ .

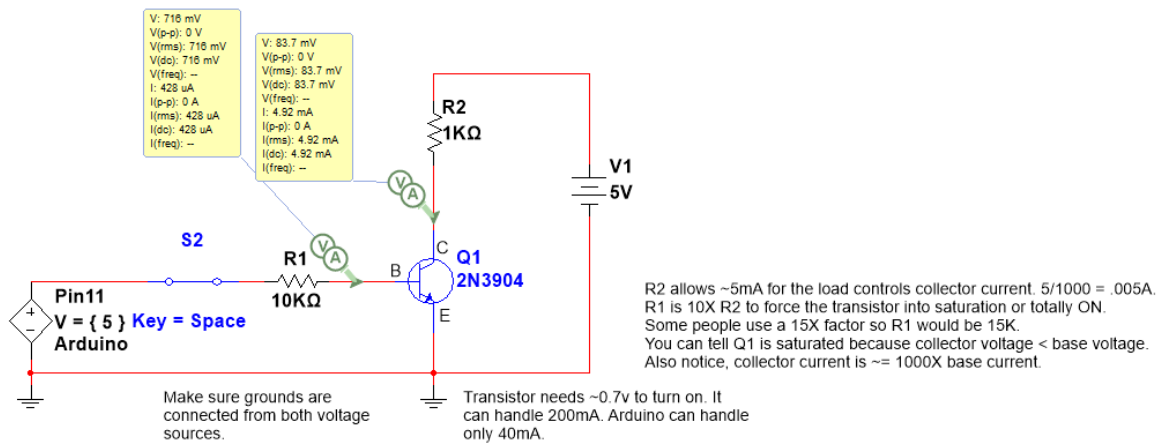- From Ohm's law, Power<sub>watts</sub> =  $I^2R$ .
- Power consumed by the  $R_{LED} = .02^2 \times 220\Omega = \underline{.09W}$ .
- So, what wattage resistor do we need? Well, since  $\frac{1}{4}$  watt = .25, that should work fine.
- Use a 220Ω  $\frac{1}{4}$  watt or  $\frac{1}{2}$  watt resistor.**



Title: STUDY GROUP LESSON 8: How to Use a Transistor as a Switch Biased for Saturation		
2N3904 Used to sink LED to ground (Q1 supplies a connection to ground or B-).		
Designed by: Ron Kessler	Document N: 1	Revision: 1
Checked by:	Date: 10/21/2022	Size: A
Approved by:	Sheet 1 of 1	

### CHARACTERISTICS

T<sub>amb</sub> = 25 °C.

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
I <sub>CBO</sub>	collector-base cut-off current	V <sub>CB</sub> = 30 V; I <sub>E</sub> = 0 A	–	50	nA
I <sub>EBO</sub>	emitter-base cut-off current	V <sub>EB</sub> = 6 V; I <sub>C</sub> = 0 A	–	50	nA
h <sub>FE</sub>	DC current gain	V <sub>CE</sub> = 1 V; note 1 I <sub>C</sub> = 0.1 mA I <sub>C</sub> = 1 mA I <sub>C</sub> = 10 mA I <sub>C</sub> = 50 mA I <sub>C</sub> = 100 mA	60 80 100 60 30	– – 300 – –	
V <sub>CEsat</sub>	collector-emitter saturation voltage	I <sub>C</sub> = 10 mA; I <sub>B</sub> = 1 mA; note 1 I <sub>C</sub> = 50 mA; I <sub>B</sub> = 5 mA; note 1	– –	200 200	mV mV

Figure 2: Partial datasheet for 2N3904 used to compute currents